
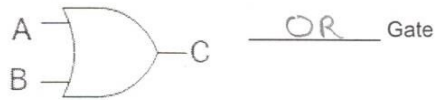


# Logic Gates Worksheet


0 = \_\_\_\_\_ 1 = \_\_\_\_\_

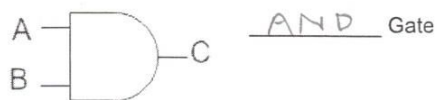


A (input 1)	B (input 2)	C (Output)
0	0	0
0	1	1
1	0	1
1	1	1



A (input 1)	B (input 2)	C (Output)
0	0	0
0	1	0
1	0	0
1	1	1

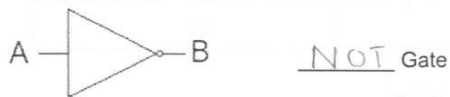

A (input)	B (output)
0	1
1	0

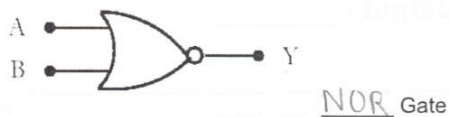


A (input 1)	B (input 2)	Y (Output)
0	0	1
0	1	0
1	0	0
1	1	0

# Logic Gates Worksheet



XOR Gate


A (input 1)	B (input 2)	Y (Output)
0	0	0
0	1	1
1	0	1
1	1	0

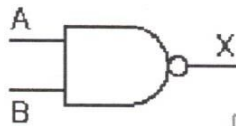

NAND Gate

A (input 1)	B (input 2)	Y (Output)
0	0	1
0	1	1
1	0	1
1	1	0
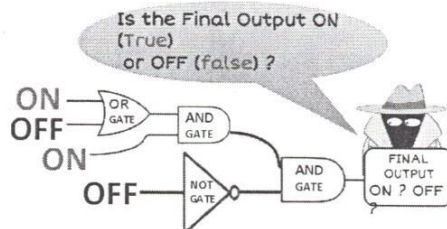
## Practice (show your work along the way)




Boolean Expressions

Gate	Symbol	Operator
And		$\cdot$
OR		$+$
NOT		$-$ NOT $\neg$ $\bar{A}$
NAND		$\cdot$
NOR		$+$
XOR		$\oplus$


# Logic Gates Worksheet
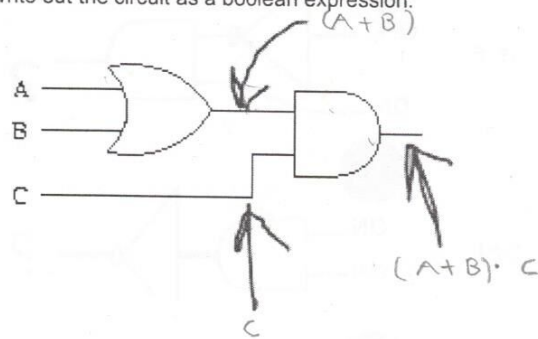
## Class Example:

Write out the circuit as a boolean expression:













Try this one:

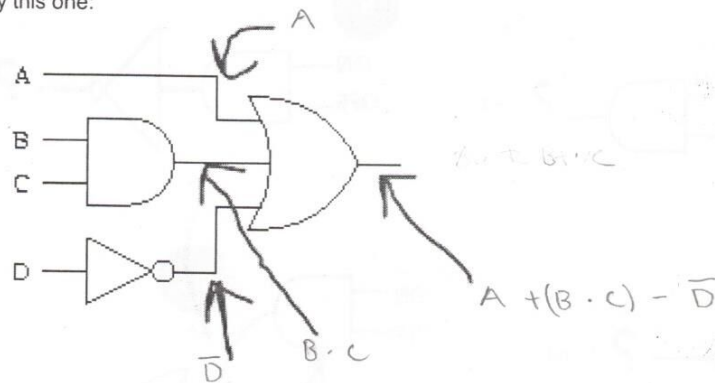


# Logic Gate Worksheet - TEJ3M


Name: \_\_\_\_\_

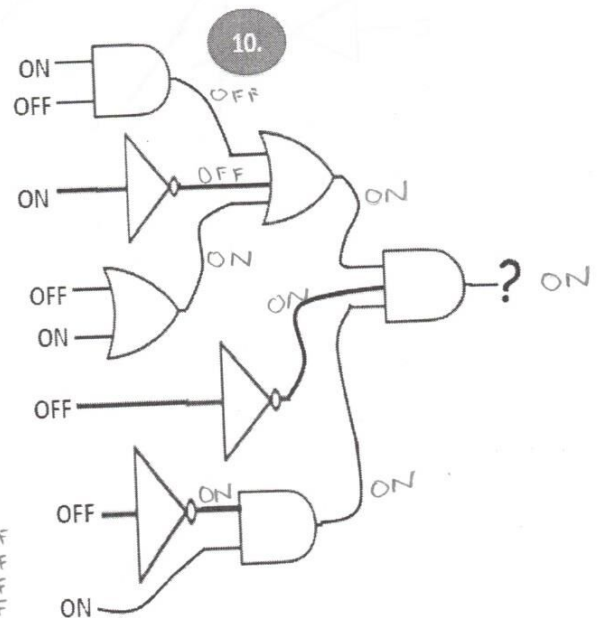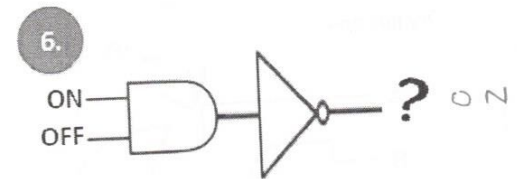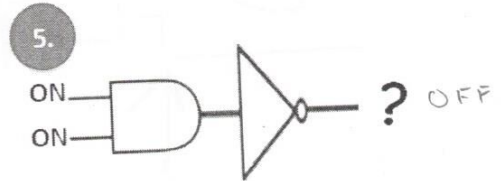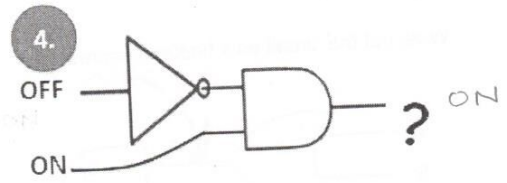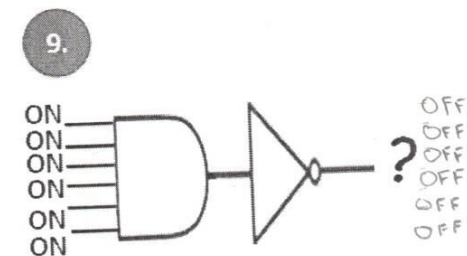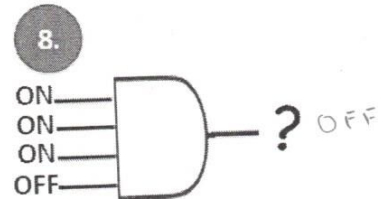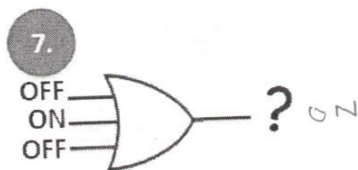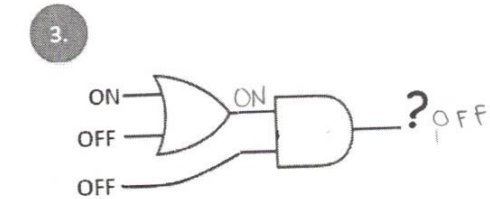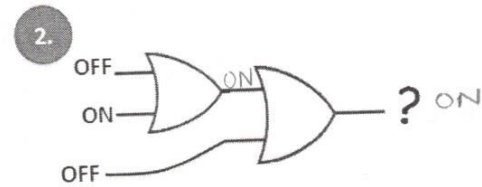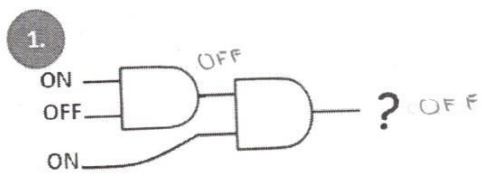

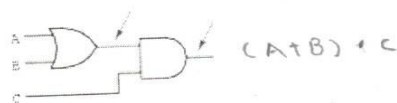
11. Convert the following logic gate circuit into a Boolean equation, writing Boolean sub-expressions next to each gate output in the diagram:



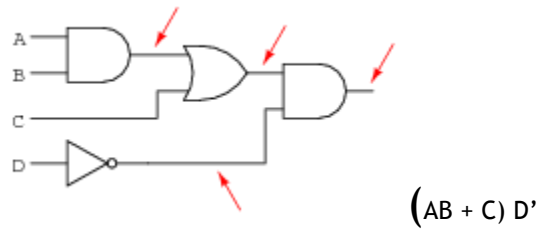12. Convert the following logic gate circuit into a Boolean equation, writing Boolean sub-expressions next to each gate output in the diagram:



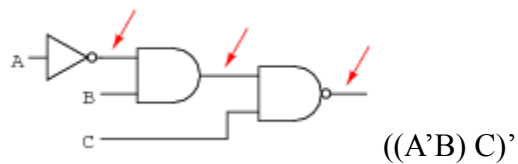
13. Convert the following logic gate circuit into a Boolean equation, writing Boolean sub-expressions next to each gate output in the diagram:




14. Draw the following logic gate circuit based on the expressions below:

$(AB + C)D$

$(AB + \underline{C})D$

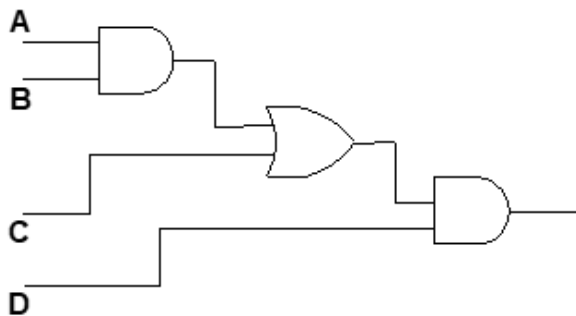

$(A + B)(B + C)$

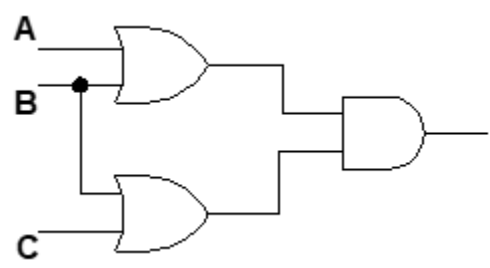

$$A'B + (B+C)'$$

