

LOGIC GATE LABS


Instructions on wiring logic gates

OVERVIEW

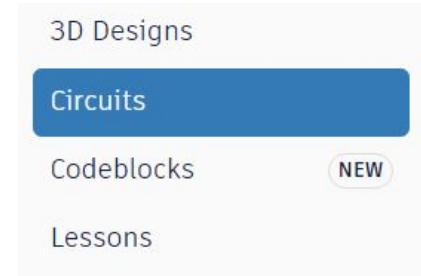1. [Tinkercad Site Login Instructions](#)
2. [AND GATE Pin Layout](#)
3. [Wiring an AND Gate](#)
4. [Other Gates](#)

LOGIN INSTRUCTIONS

- Go to <https://www.tinkercad.com/login>
- Use the account you used just before the March Break when you registered and created your profile.
- Make sure that circuits is selected



- To begin the lab assignments click on


A green rectangular button with rounded corners and a thin white border. The text 'Create new Circuit' is written in white, sans-serif font, centered on the button.

Create new Circuit

POWER

- All chips need power
- Pin 14 is VCC you need to connect 5v to this pin

Connect to +6v

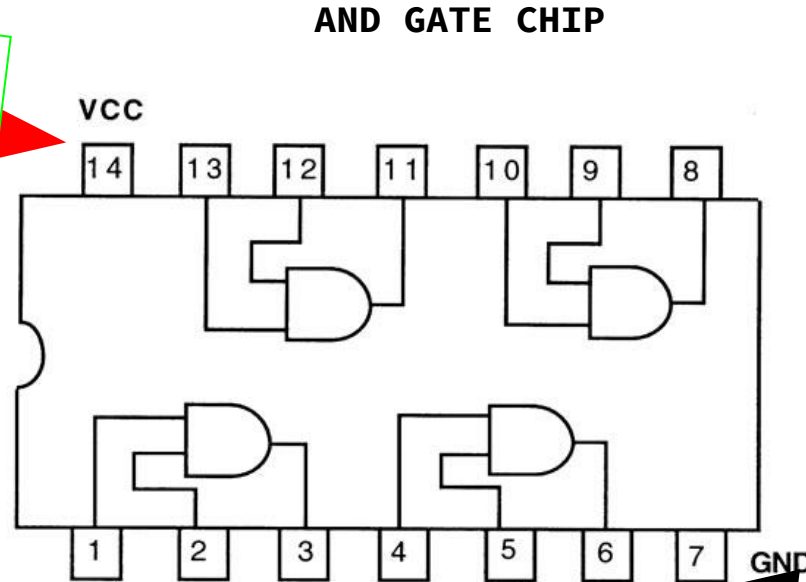


74LS08


Connect to 0v (Gnd)

- Pin 7 is Gnd, you need to connect the 0v to this pin

INITIAL SETUP

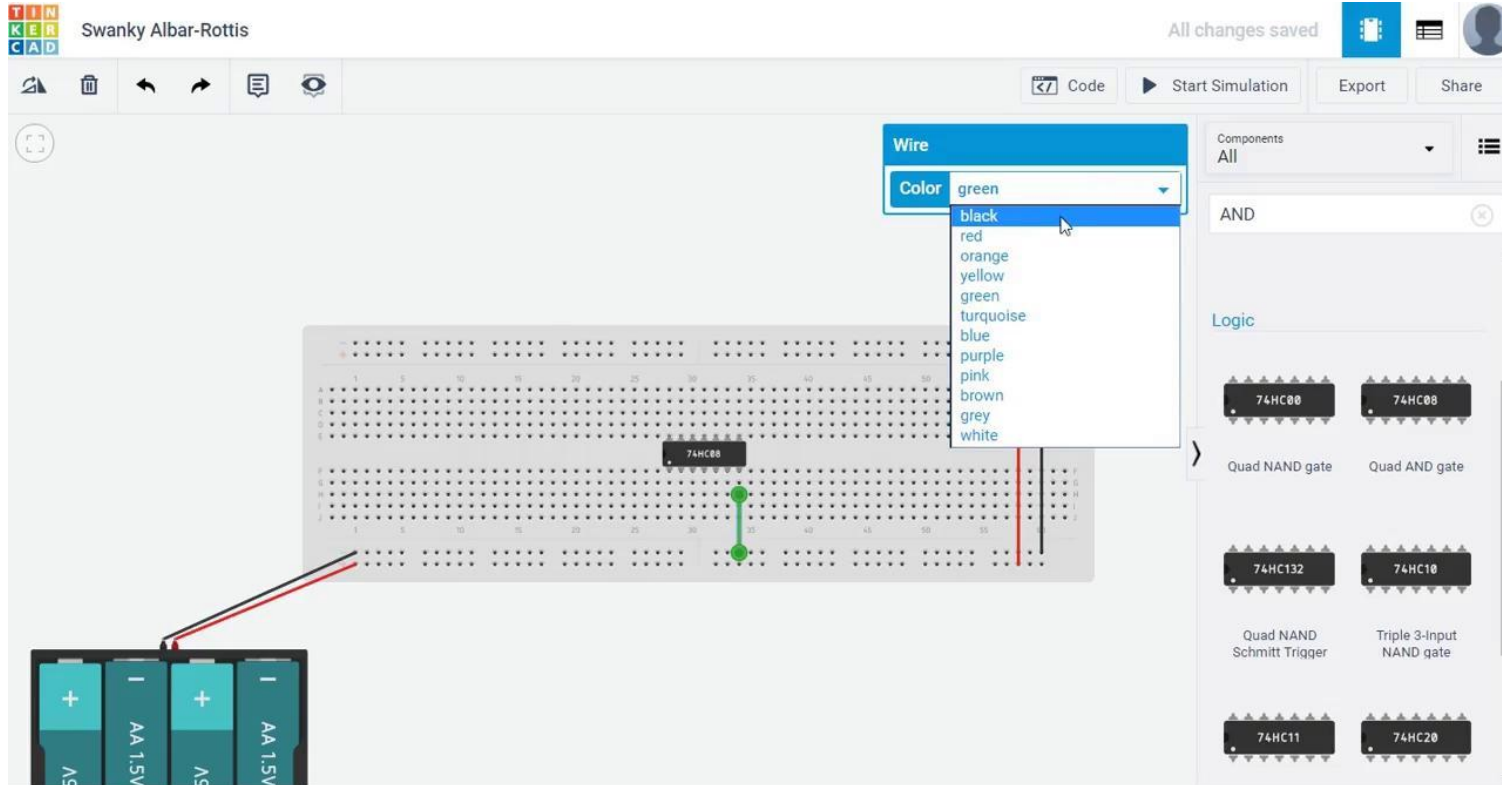


WIRING THE AND GATE

 


For more information on DIP switches, go here:

<https://www.computerhope.com/jargon/d/dipswitc.htm>

WIRING THE LED AND TESTING THE CIRCUIT

 

FINAL CIRCUIT

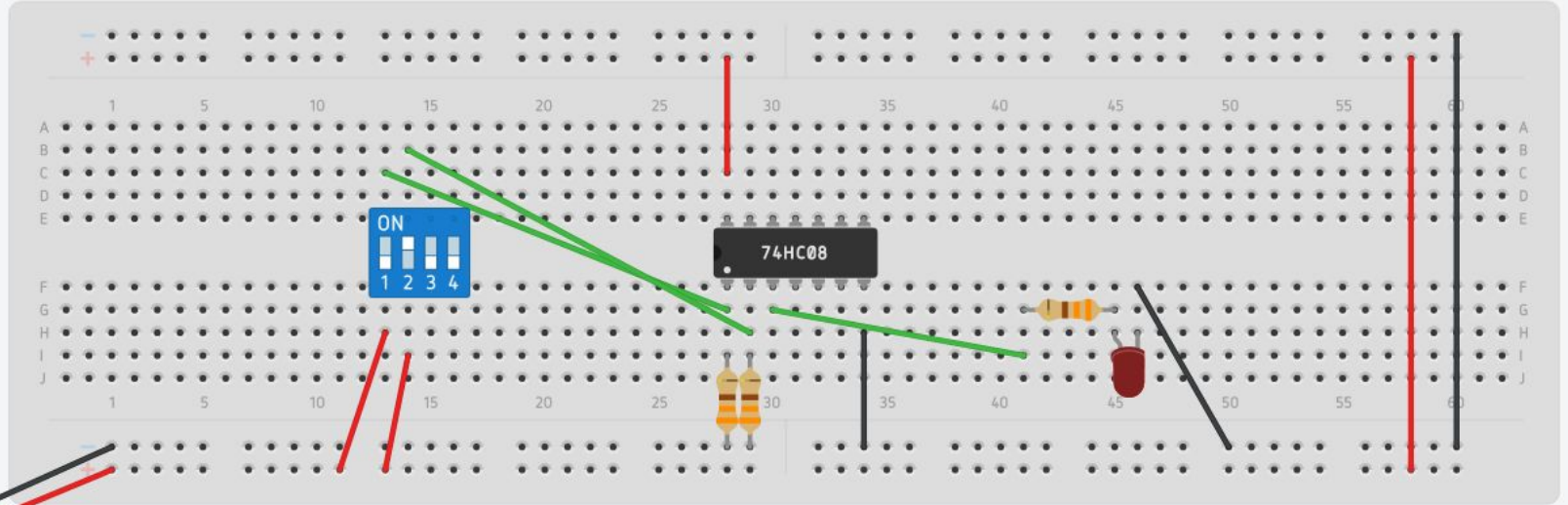

OTHER GATES


NAND gate (S00)

OR Gate (S32)


NOR Gate (S02)

XOR gate (S86)


NAND GATE

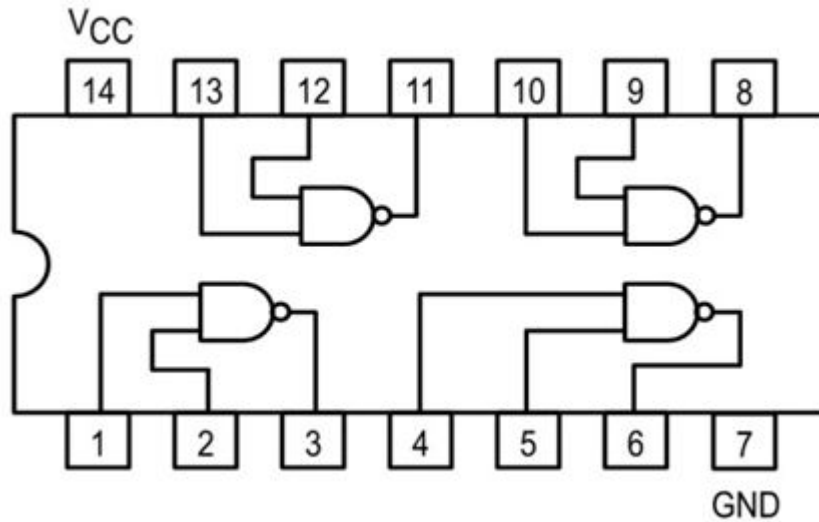


OR GATE

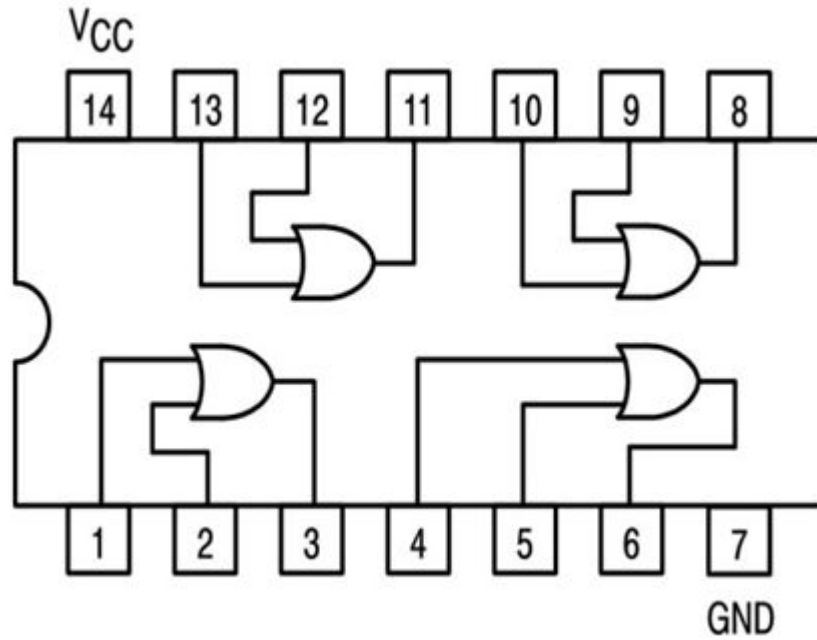

NOR GATE

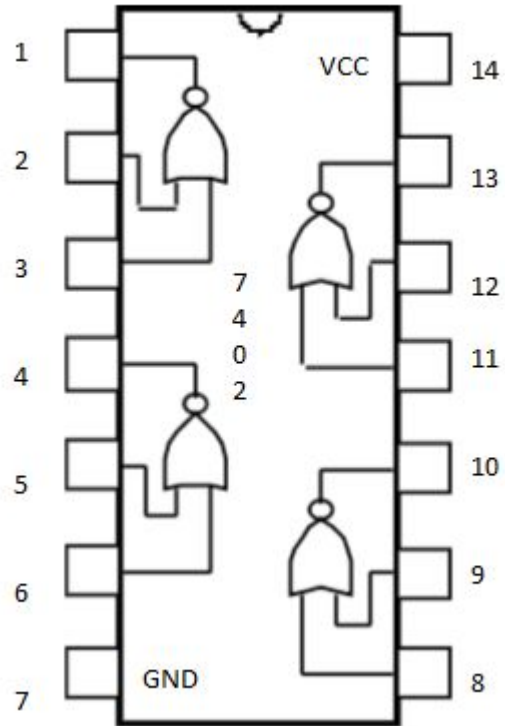

XOR GATE

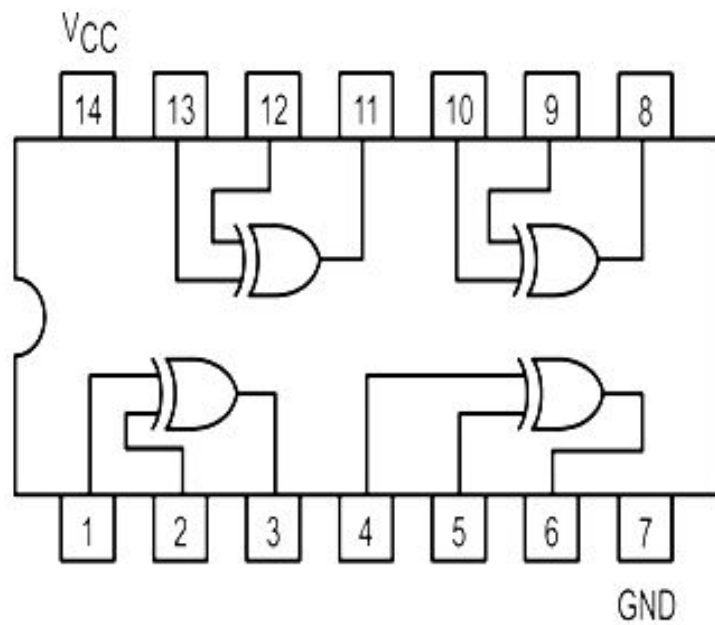

THIS WEEK...

- Work on new lab
- Other logic gate labs will be posted this week but for now, I will only post 1
- Finish up labs from last week if you are not already finished.
- We will be doing a summative based on this week's work so make sure you keep up and ask questions if you having difficulty.