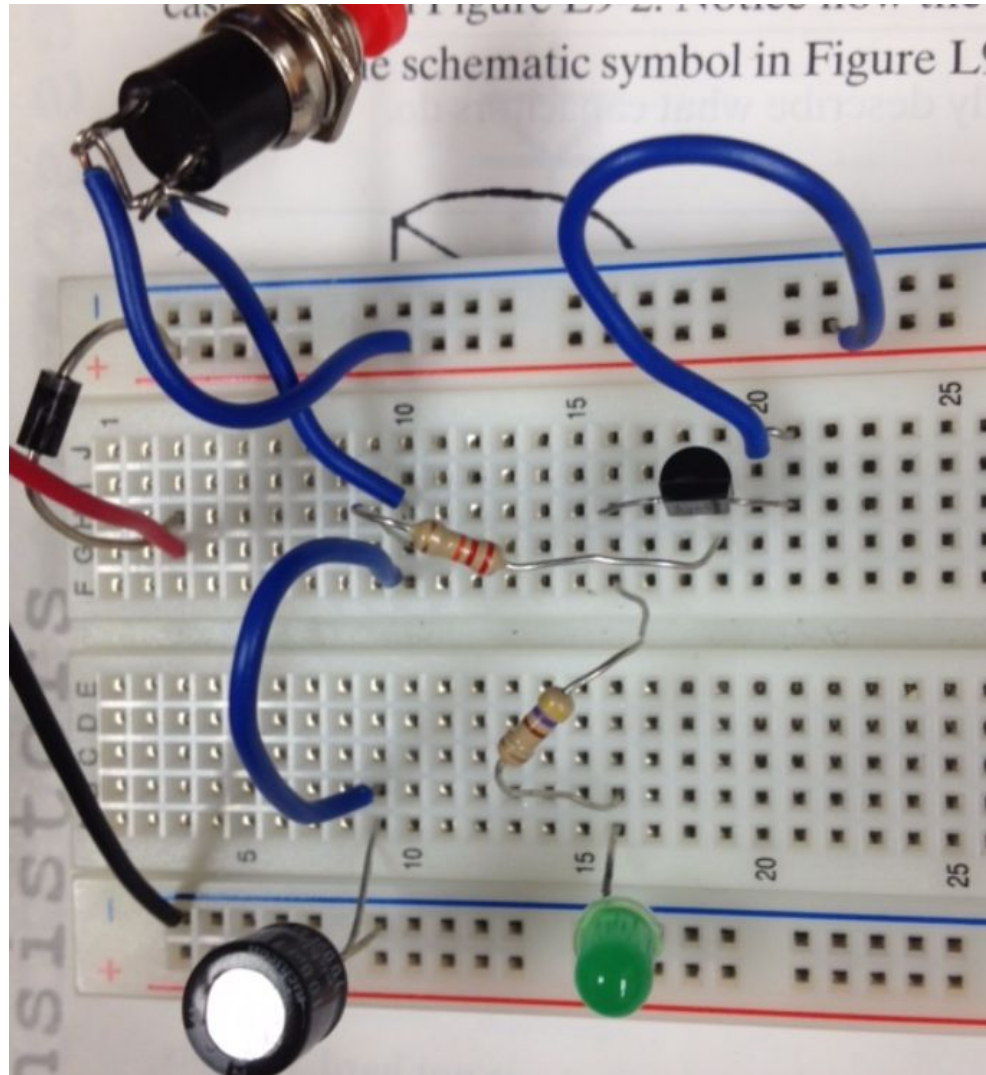


Introduction to Electricity/ Electronics




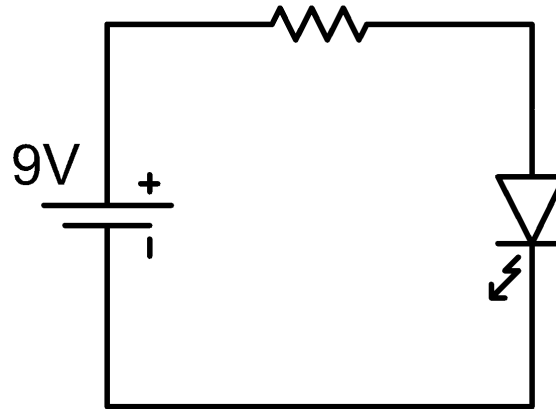Example of a circuit



What's an Electrical Circuit?

- Every circuit requires these three things:
 - Power Source
 - Load
 - Conductor



- Optionally, a circuit may include a “control device” such as a switch



Three Main Invisible Quantities

- **Voltage** - Provides the “push”
symbol - **V**, units - **Volts**
- **Current**,
 - Flow of Electrons
 - Amount of Current is dependent on Voltage and Resistance
symbol - **I**, units - **Amperes (Amps)**
1 Amp = 6.24×10^{18} electrons move through a wire every second
- **Resistance**
 - Limits the amount of current
 - Represents the “load” of the circuit
symbol - **R**, units - **Ohms (Ω)**

Unit Name	Unit Symbol	Quantity
Ampere (amp)	A	Electric current (I) 1 Amp = 6.24×10^{18} electrons move through a wire every second
Volt	V	Voltage
Ohm	Ω	Resistance (R)
Farad	F	Capacitance (F)

Ohm's Law

“Current (I) is proportional to Voltage (V) and inversely proportional to Resistance (R)”

$$I = \frac{V}{R}$$


$$V = I \times R$$

$$R = \frac{V}{I}$$

Prefix	Prefix Symbol	Prefix factor	Example
nano	n	10^{-9}	$1\text{nF} = 10^{-9}\text{F}$
micro	μ	10^{-6}	$1\mu\text{A} = 10^{-6}\text{A}$
milli	m	10^{-3}	$1\text{mA} = 10^{-3}\text{A}$
kilo	k	10^3	$1\text{k}\Omega = 1000\Omega$
mega	M	10^6	$1\text{MHz} = 10^6\text{Hz}$
giga	G	10^9	$1\text{GHz} = 10^9\text{Hz}$

Waterfall Analogy

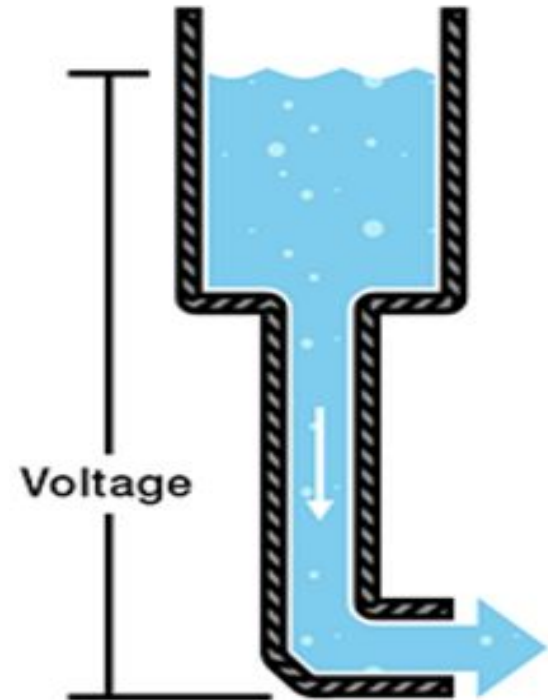- The voltage is equivalent to the water pressure, the current is equivalent to the flow rate, and the resistance is like the pipe size.
- Water = Charge
- Pressure = Voltage
- Flow = Current



Types of Electricity




Direct Current (DC)

- Batteries, fuel cells and solar cells all produce something called **direct current** (DC).
- The positive and negative terminals of a battery are always, respectively, positive and negative.
- Current always flows in the same direction between those two terminals.

Voltage Can Be Provided From...

- A battery - DC (Direct Current)

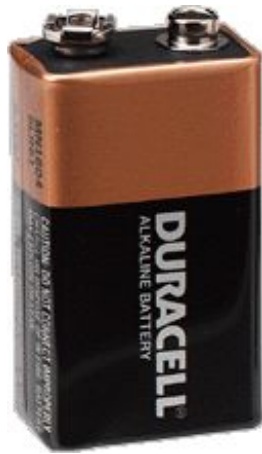

Alternating Current (AC)


- The power that comes from a power plant, on the other hand, is called **alternating current (AC)**.
- The direction of the current reverses, or alternates, 60 times per second
- The power that is available at a wall socket in Canada is **120-volt, 60-cycle AC power**

AC Cont'd

- Home and office outlets are almost always AC because generating and transporting AC across long distances is easy (using transformers)
- capable of powering electric motors (converting electrical energy into mechanical energy) – useful for dishwashers and refrigerators which run on AC

Voltage Can Be Provided From...

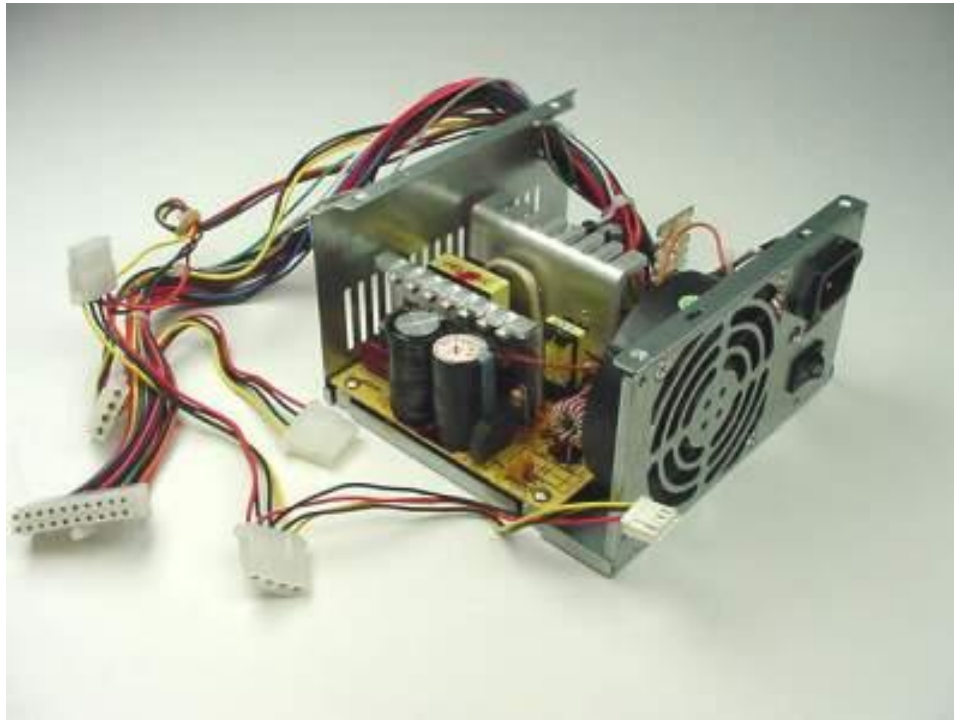- Computer Power Supply or Electrical Point on the wall – AC (Alternating Current)




- Red: 5V
- Yellow: 12V
- Black: Ground

Current


- ...is simply the flow of electrons
- Direction depends on convention

■ Electron flow is from (-) to (+) (*flow of electrons*)

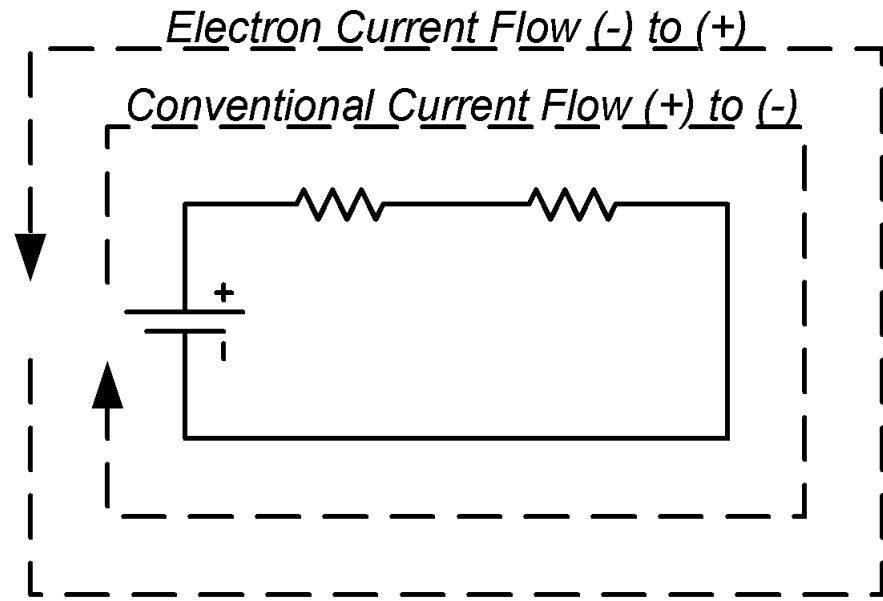■ Conventional flow is from (+) to (-) (*hole flow*)




Resistors – Basic Specs



- Can be rated by...
 - Resistance (Ohms, Ω)
 - Tolerance (% of nominal value)
 - Power Rating (Watts)
- Schematic Symbol... 

Resistors – Types

- Fixed

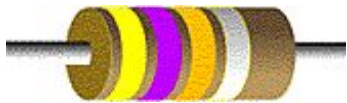

- Variable (Potentiometer, Rheostat)

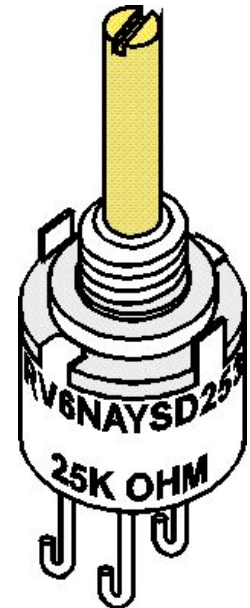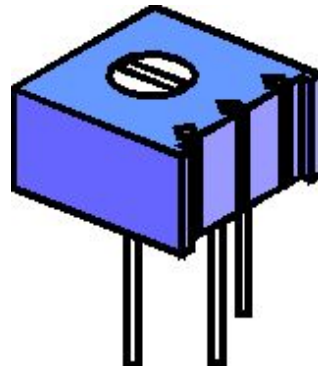

Resistors - Types

LDR (Light Dependant Resistor)


- The resistance changes as intensity of light changes

-

Cadmium
Sulphide Track



Symbol


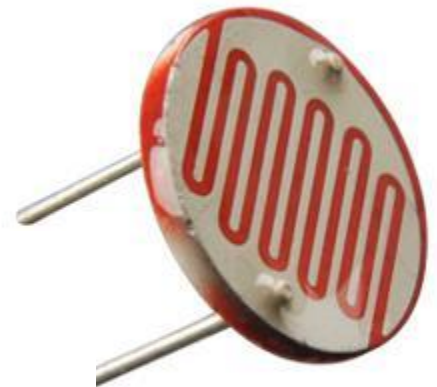


Capacitors

- **Capacitors store charge,**
- **Pass high frequencies, and**
- **Block DC**

Measured in Farads, Usually in microfarads


SYMBOL

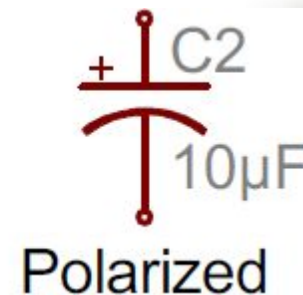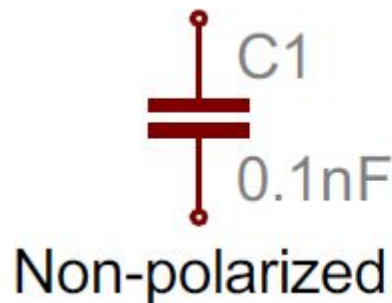

Diodes



- *restricts current in one direction*
- *Some give out light (LED)*
- *Others maintain fix voltage*

SYMBOL

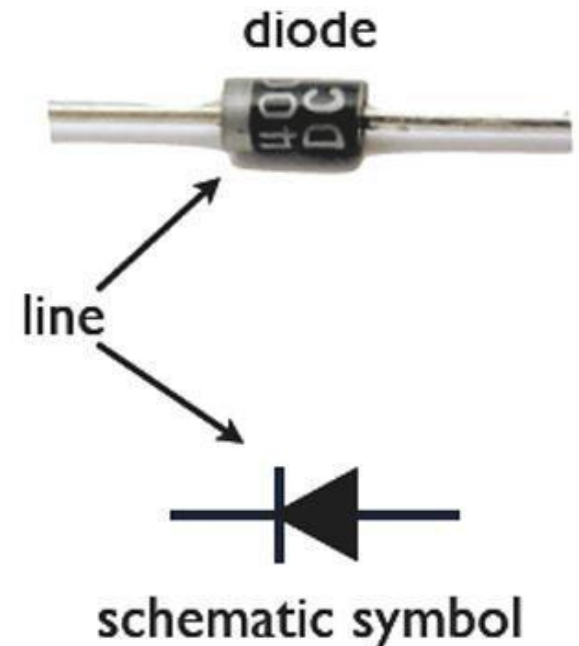

Light Emitting Diodes

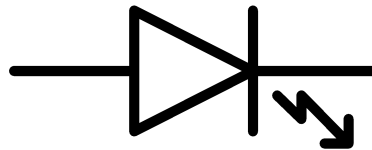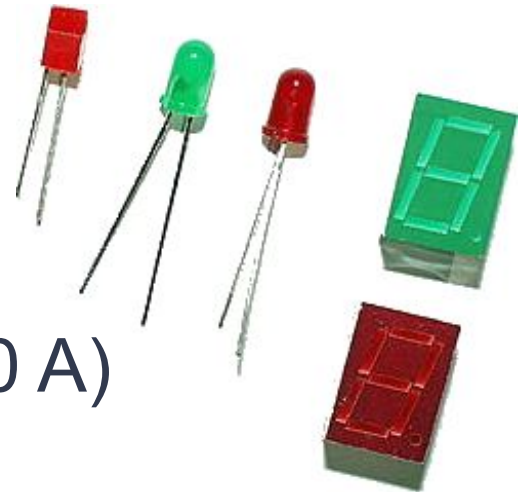- A type of diode designed to emit light
- Can be visible or IR
- 2 V voltage drop
- Typically draws 20 mA (0.020 A)
- Schematic Symbol...




Grounding Circuits



- Ground in the power-distribution grid is literally "the ground" that's all around you when you are walking outside.
- Remember, all circuits must complete the path by returning to the positive side of the source.
- A ground completes all circuits by “grounding” the flow of electrons after they have done their job.

RESISTORS – COLOUR CODES

Example: 4K7 or 4700 ohms (Carbon)

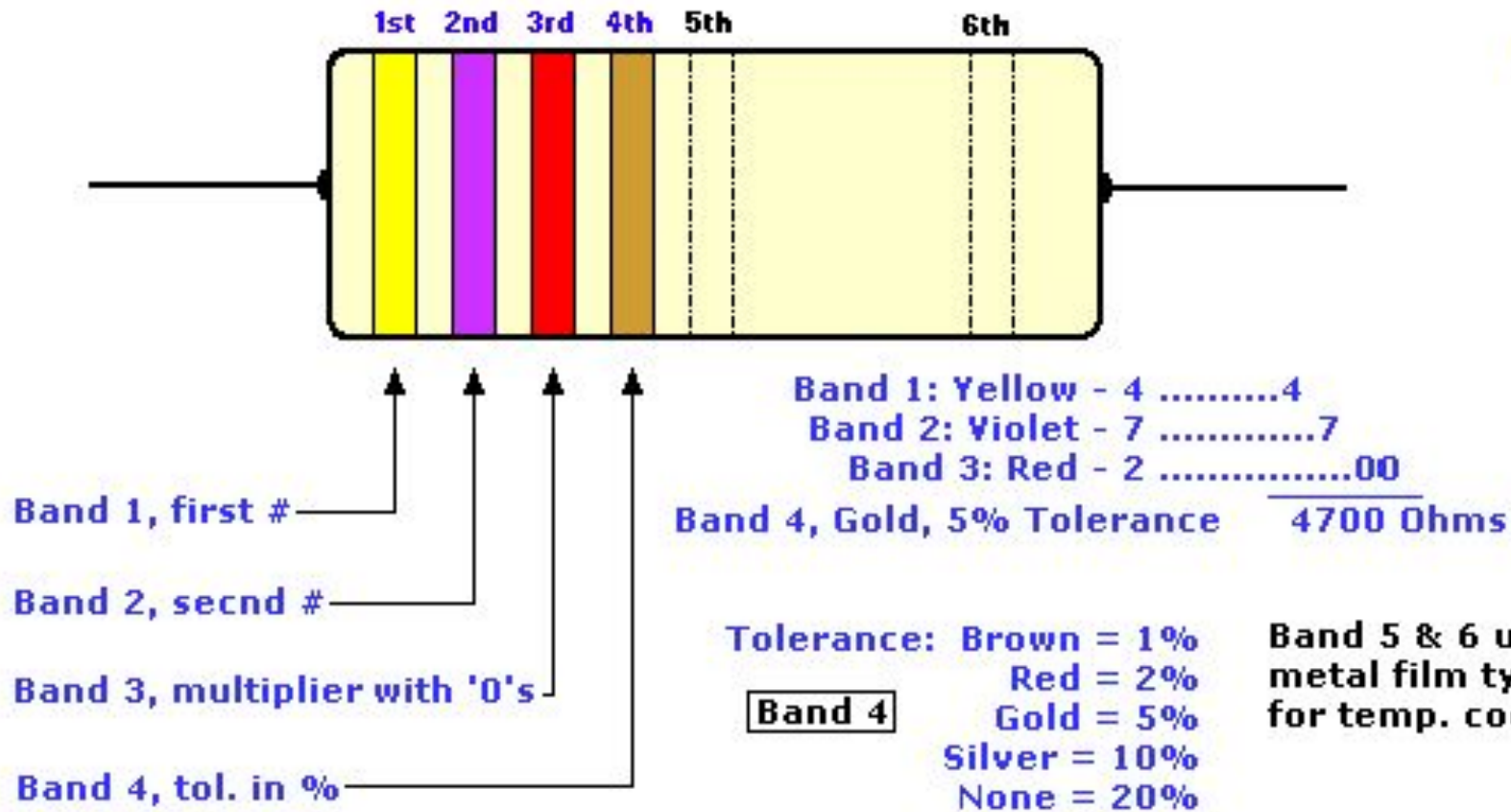

Band 1, 2, 3	
Black	= 0
Brown	= 1
Red	= 2
Orange	= 3
Yellow	= 4
Green	= 5
Blue	= 6
Violet	= 7
Gray	= 8
White	= 9
Gold	= 0.1

Tolerance:	
Brown	= 1%
Red	= 2%
Gold	= 5%
Silver	= 10%
None	= 20%

Band 4

Band 5 & 6 usually for 1% metal film types. Band 6 for temp. coefficient.




0		Black
1		Brown
2		Red
3		Orange
4		Yellow
5		Green
6		Blue
7		Purple
8		Grey
9		White

$\pm 5\%$		Gold
$\pm 10\%$		Silver

Color Codes

Brown	$\pm 1\%$
Red	$\pm 2\%$
Gold	$\pm 5\%$
Silver	$\pm 10\%*$

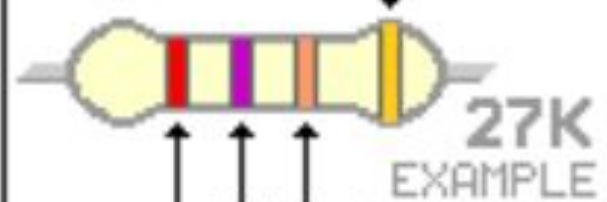


0	X1
1	X10
2	X100
3	X1000
4	X10000
5	X100000
6	X1000000
7	$\div 10$ Gold
8	$\div 100$ Silver
9	

4 Band Resistors

Color	Digit	Multiplier	Tolerance (%)
Black	0	10^0 (1)	
Brown	1	10^1	1
Red	2	10^2	2
Orange	3	10^3	
Yellow	4	10^4	
Green	5	10^5	0.5
Blue	6	10^6	0.25
Violet	7	10^7	0.1
Grey	8	10^8	
White	9	10^9	
Gold		10^{-1}	5
Silver		10^{-2}	10
(none)			20

RESISTORS EXAMPLE

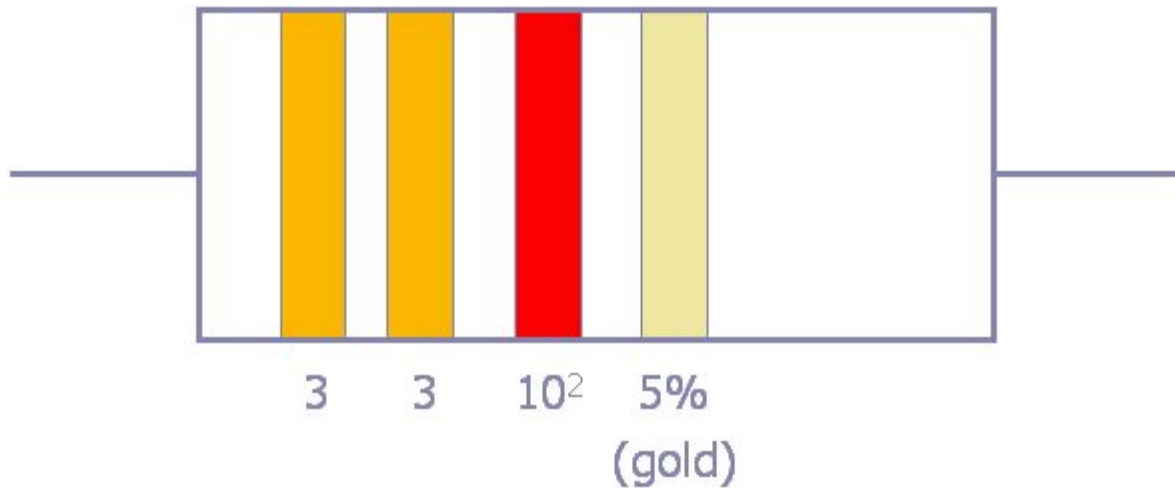

1st band: orange = 3

2nd band: orange = 3

3rd band: red = 2 (i.e. 10²)

4th band: gold = 5%

$$\begin{aligned} 33 \times 10^2 \\ &= 3300 \, \Omega \\ &= 3.3 \, \text{k}\Omega \end{aligned}$$

Work on the Resistor Worksheet
handout

20 questions in total